

SUMMER PROJECT REPORT

Course: MEL G642

Date: 10th June 2023

Name: VLSI Architecture Design

Sem: 2nd / HD

Submitter Detail:

Bharathi Shrinivasan T R

2022H1400182P (M.E. Embedded Systems)

Objective: Understand and comprehend the design philosophy of CISC based Processor architecture.


Reference: "Microprocessor Logic Design: Flowchart Method" - Nick Tredennick

Project:

1. Learn flowchart method-based development of CISC architecture design.
2. Develop a custom 16-bit MIN (Minimum) architecture prototype using HDL modelling of the logic circuits and implementing same on Xilinx's ZedBoard (Zynq 7000 series FPGA).
3. Machine-code a program to compute Fibonacci series using the implemented processor.

Project database links:

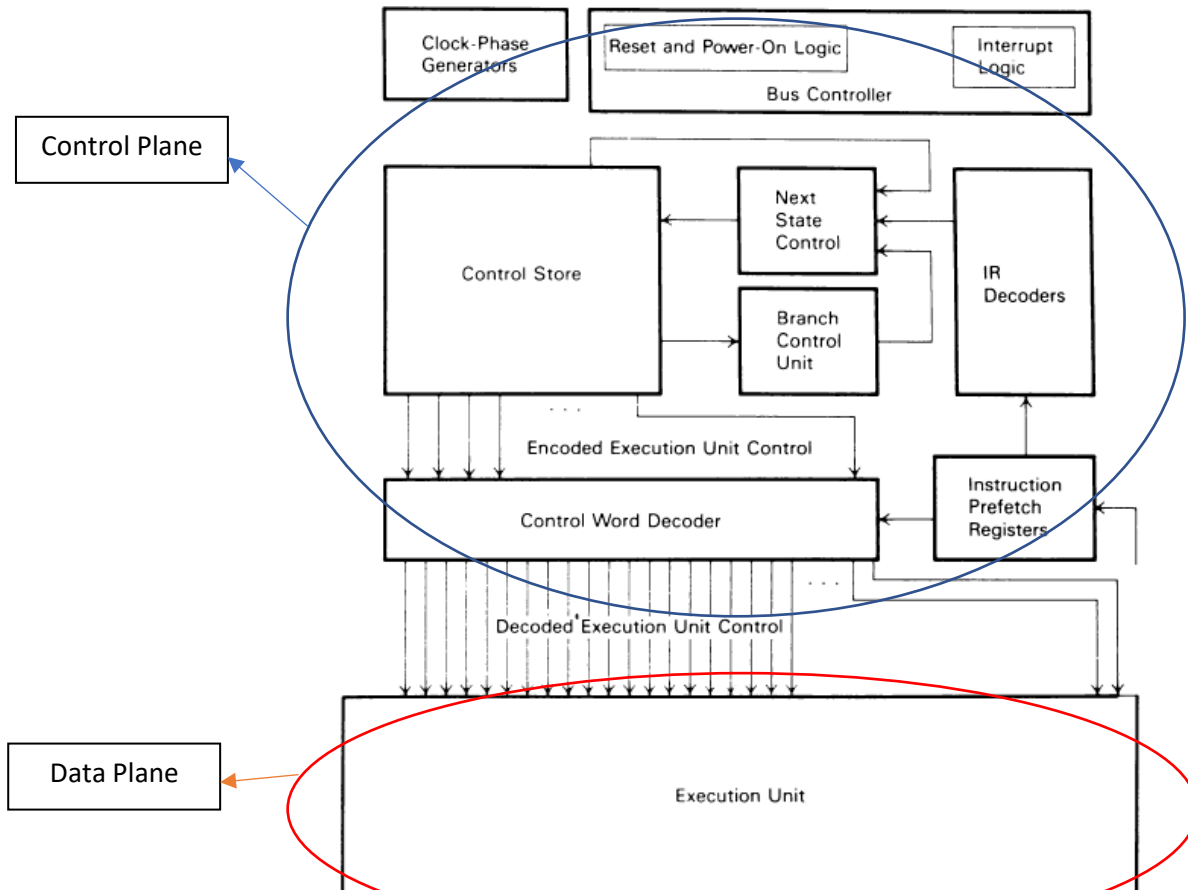1. Complete Vivado (2020.2) source code file: [Drive Link](#)
2. Simulation results and report: [Drive Link](#)




1.1 Block diagram of a complete CISC architecture

Table of Contents

Design Workflow carried out during this project	3
Programmer's Instruction format and list of supporting instructions	4
Control Word Format -	5
Decoded control word format used by Execution Unit –	5
DATA Plane development.....	6
Programmer's Register Bank:	6
Simple Register module:.....	6
ALU design:	7
External Memory Unit:	7
Complete Execution Unit:.....	7
Flow chart used in the project / CISC micro-code:	8
Testing Data path using vivado simulation –	9
Control Plane Development –	10
Instruction Decoder Unit-.....	10
Next State Logic Unit –	11
Control Store Unit-.....	12
Testing Control Plane using Vivado Simulation –	13
Overall Unit integration and RTL analysis –	14
Testing Programmer's instruction –	15
Appendix –	17
Decoder Control Word discussion –	17
Execution Unit discussion –	18
Next State logic discussion –	19
Clock Phase discussion –	20
Fibonacci result –	20
Overall MIN architecture simulation –	21

Design Workflow carried out during this project

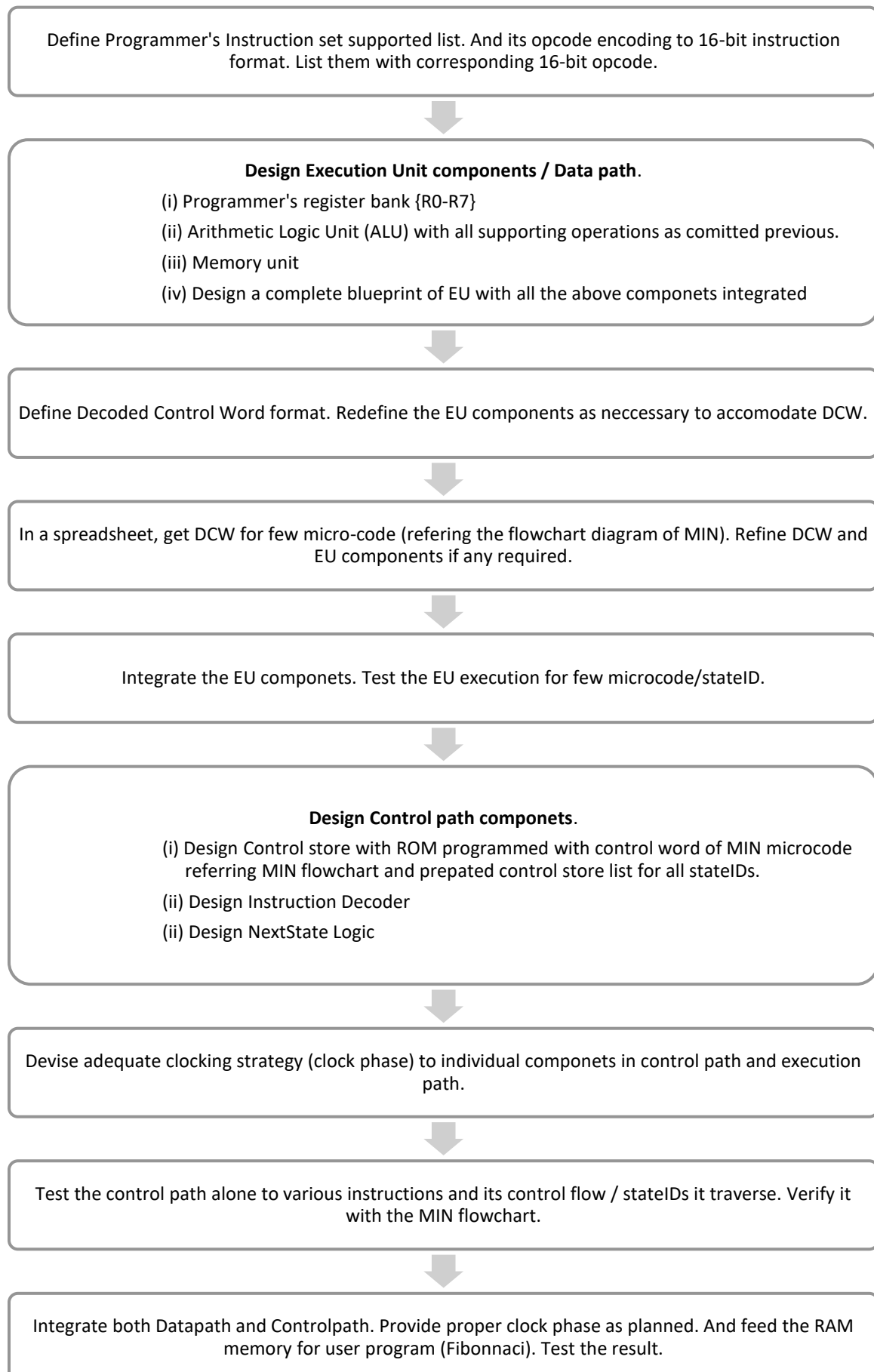The Design of microprocessor majorly has two phase – Data-path design, Control-path design. This section shows the water-flow model of the work carried in this complete design.



Programmer's Instruction format and list of supporting instructions

Programmer's Instruction	Operation
NOP	No Operation: No change in Reg/MEM/flag.
LDR Rx,Ry	Load: Rx <- Ry , Indirect mode Rx<-@Ry
STR Rx,Ry	Store: Rx->Ry, indirect mode Rx->@Ry
TST Ry	Test: @Rx is read in ALU and only flags are modified. No change in Reg/MEM/flag.
BZ Ry	If flag is Zero jumps to Ry pointing instruction. No change in Reg/MEM/flag.
ADD Rx,Ry	Add: Ry<-Rx+Ry
SUB Rx,Ry	Subtract: Ry<-Rx-Ry
AND Rx,Ry	Bitwise AND: Ry<-Rx&Ry
OR Rx,Ry	Bitwise OR: Ry<-Rx Ry
XOR Rx,Ry	Bitwise XOR: Ry<-Rx^Ry
PUSH Rx,Ry	Ry<-Ry-1, @Ry<-Rx (Fully Decending stack)
POP Rx,Ry	Rx<-@Ry, Ry<-Ry+1 (Fully Decending stack)

Each instruction is 16-bit in width, bit field anatomy is given as below. The supported list of programmer's instruction along with custom assigned Op-Code is listed in the above figure.

	15-12	11-10	9-8	7	6-4	3	2-0
Programmer's	4-bit	2-bit	2-bit	1-bit	3-bit	1-bit	3-bit
Instruction	Op Code	Future	Mode	Future	Rx	Future	Ry
NOP	0	0	00: direct	0	R0	0	R0
LDR	1	0	01: indirect	0	R1	0	R1
STR	2	0	10: indirect+base	0	R2	0	R2
TST	3	0		0	R3	0	R3
BZ	4	0		0	R4	0	R4
ADD	5	0		0	R5	0	R5
SUB	6	0		0	R6	0	R6
AND	7	0		0	R7	0	R7
OR	8	0		0		0	
XOR	9	0		0		0	
PUSH	10	0		0		0	
POP	11	0		0		0	

Reference –

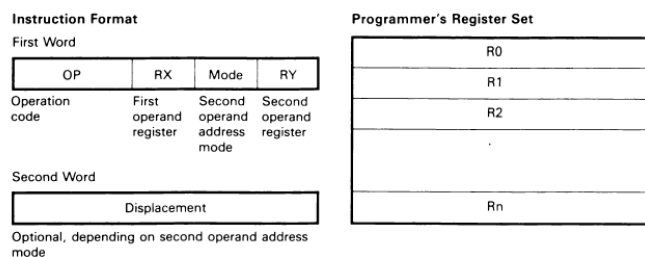


Figure 3.2 MIN instruction format and register set

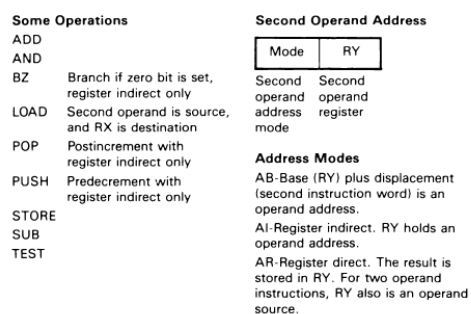


Figure 3.3 MIN instruction set summary

Few examples of instructions and it's opcode -

Instruction	OpCode (Hex)
LDR R5,R7	16'h1057
LDR R4,[R5]	16'h1145
LDR R6,[R7+10]	16'h1267 16'h000A
BZ R6	16'h4006

The Op-code- 1st nibble corresponds to the operation/instruction, 2nd nibble is the addressing mode, 3rd is Rx selection, 4th is Ry selection.

Note: for Indirect addressing plus displacement mode, the Opcode generated is 16+16bits / 4byte long – the first 2byte is the instruction opcode, second 2byte is the displacement value.

Control Word Format -

Control Word		
26 bits	2 bits	6 bits
Decoded Control Word	TY selection	Next Address

The Control Store contains Control Word for each State-ID. Note, in this architecture we didn't use a dedicated Control Word decoder unit, so the ready decoded control word is stored in Control Word itself. The bit size and field anatomy is as above.

Decoded control word format used by Execution Unit –

		bit_IreIrf	bit_SrcAO	bit_WriteDO	bit_DesEdb	bit_SrcABus	bit_SrcBBus	bit_SrcRx	bit_SrcRy	bit_SrcT2	bit_SrcPC	bit_2ndOperand	bit_IntExtOp	bit_flagUpdate	bit_T1Update	bit_EnableALU
bit position ->		25	23:24	22	20:21	17:19	14:16	12:13	10:11	8:9	6:7	4:5	3	2	1	0
No of bits ->		1	2	1	2	3	3	2	2	2	2	2	1	1	1	1
	State ID	IRF->IRE	Memory Operation			Src-> A Bus	Src-> B Bus	Bus Destination				ALU Operation				
			Src-> AO	A->DO	MEM->dest			Rx	Ry	T2	PC	2nd Operand	Int/Ext Operation	UpdateFlag	UpdateT1	EnableALU
ControlStore_A ddress	XXXX	0	A->AO : 01 B->AO : 10 None : 00		edb->DI : 01 edb->IRF : 10 None : 00	Rx->A : -001 Ry->A : -010 T1->A : -011 T2->A : -100 PC->A : -101 None : 000	Rx->B : -001 Ry->B : -010 T1->B : -011 T2->B : -100 PC->B : -101 DI->B : -110 None : 000	A->Rx : 01 B->Rx : 10 None : 00	A->Ry : 01 B->Ry : 10 None : 00	A->T2 : 01 B->T2 : 10 None : 00	A->PC : 01 B->PC : 10 None : 00	B->ALU : 00 +1->ALU : 01 -1->ALU : 10 0->ALU : 11	External : 1 Internal/ADD : 0			
0	NOP	0	00	0	00	000	000	00	00	00	00	00	0	0	0	0

The above format is used in the project. The decoded control word is of 26-bit wide. The detail anatomy of each bit-field and its relation is provided.

Reference -

Control Fields										
AO	PC	T2	Regs	T1	ALU	K	DI	DO	IRE	IRF

Further note, each micro-code/StateID is executed by the EU as 3 stage-


1. Buffer the bus with its coded source. (*Src->A Bus, Src->B Bus*)
2. Registers to latch the coded bus data, Perform ALU, Perform MEM address out. (*Bus destination*)
3. Read MEM data (*MEM -> reg*)

The EU execution is clocked by 3 phase clocks for each 3 stages.

DATA Plane development


The Data path encompasses the whole Execution Unit, covering the ALU, MEM, Register Bank.

Programmer's Register Bank:

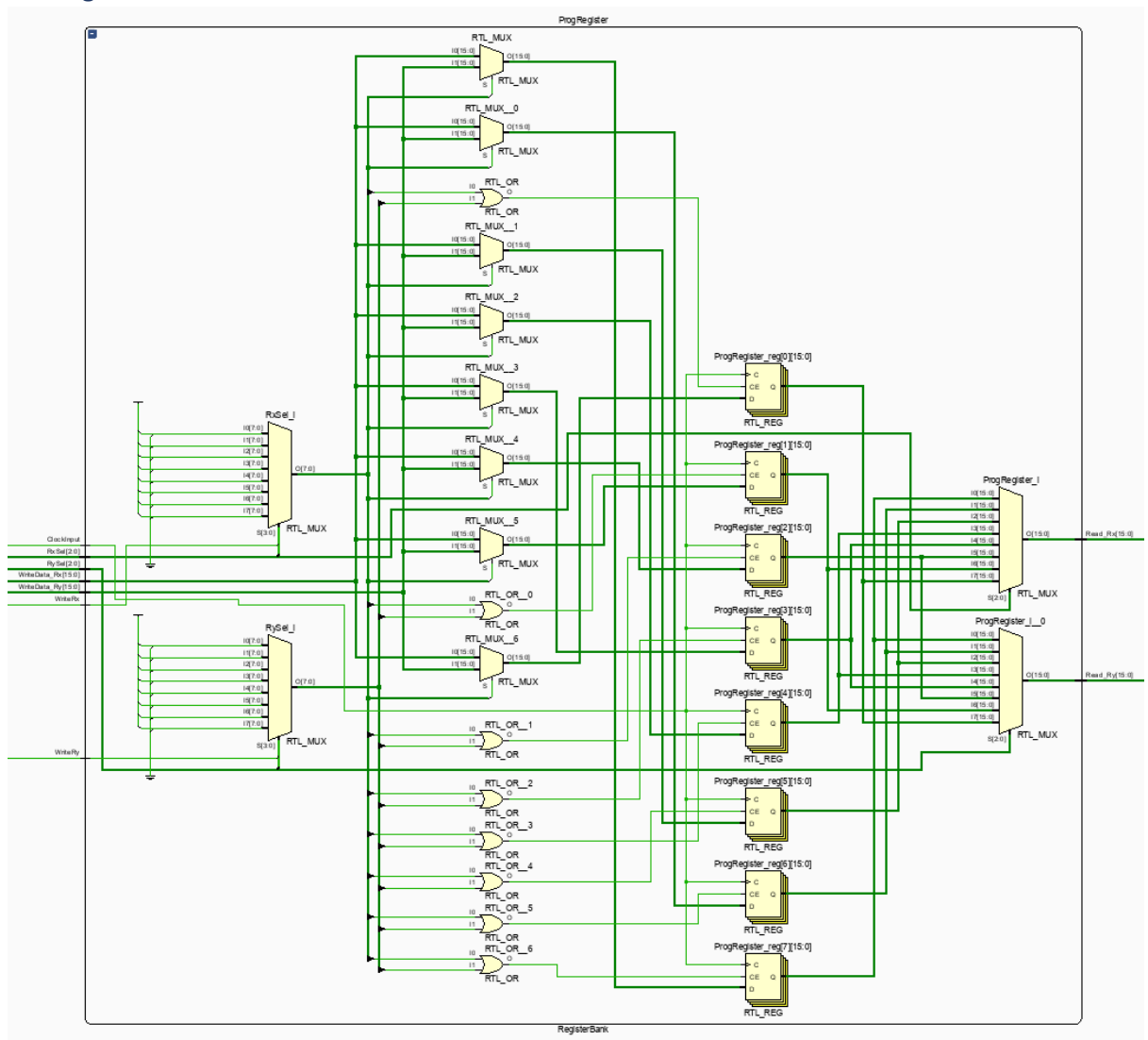

The Bank contains 8 (16-bit) registers R0-R7. Depending on the selected Rx, Ry, the corresponding registers can be independently accessed and written.


Simple Register module:

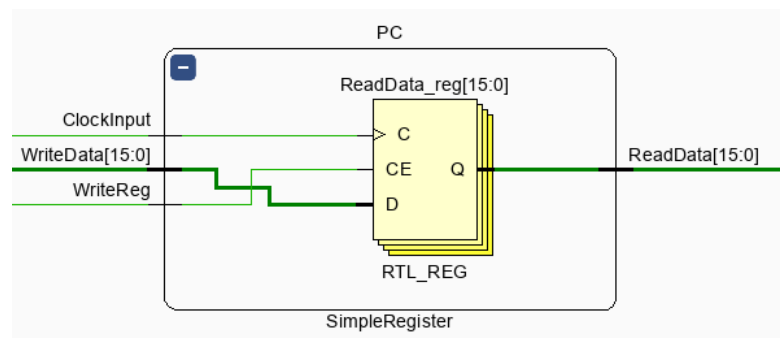


A 16-bit register with write signal gated. Used for internal registers – PC, T2, DI, DO, AO etc.,

ALU design:

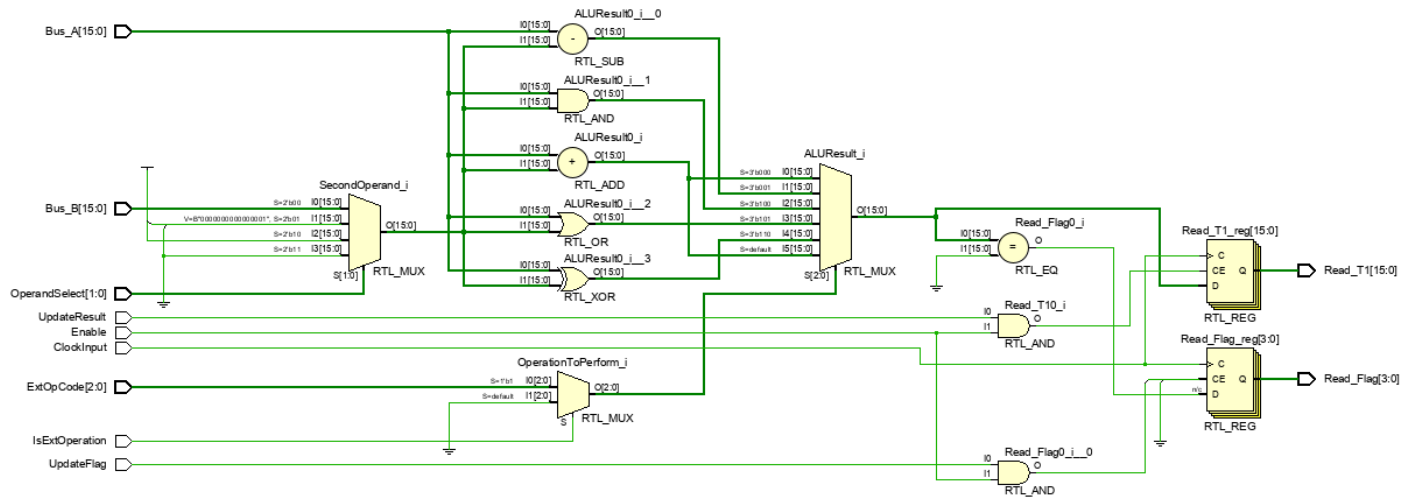- ADD, SUB, AND, OR, XOR are the instructions supported
- Condition code contains Zero flag only. (Future extendable to NEG, OV etc.,)
- ALU operates on 16-bit operand (precisely two), and yields result and condition flags.
- The ALU result is conditionally written into T1 register, condition code is conditionally written into Flag bits.



External Memory Unit:

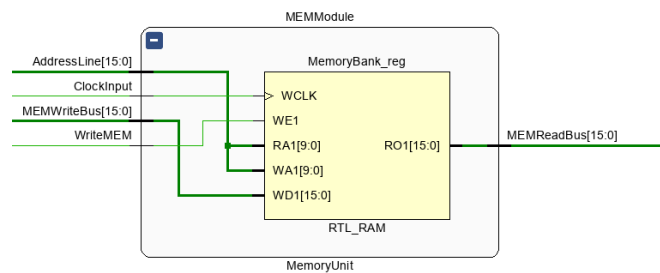

This memory contains both the Program/code and Data segment together. The MIN architecture is Princeton architecture, both the code and data are from same memory/bus.

The user program is fed into this memory. Any external read/write is done to this unit.

Complete Execution Unit:


All the registers have window to read/write into two BUS (namely Bus A, Bus B). The writing is exclusive and governed by the microcode. Further EDB and EAB connects the EU to an external Memory Unit.

Note, each micro-code is executed within as a sequence –

1. The EU buses are wetted with the register content. (i.e., Rx->a, DI->b)
2. The destined registers read the new content from designated bus line. (i.e., A->PC, B->Rx,A->AO)
3. Finally, the memory related operation is performed. (i.e., EDB->DI, EDB->IRF, DO->EDB)

The EU is developed in vivado HDL (Verilog) and the elaborated design schematic is attached in the appendix.


The complete circuit RTL analysis is given in appendix.

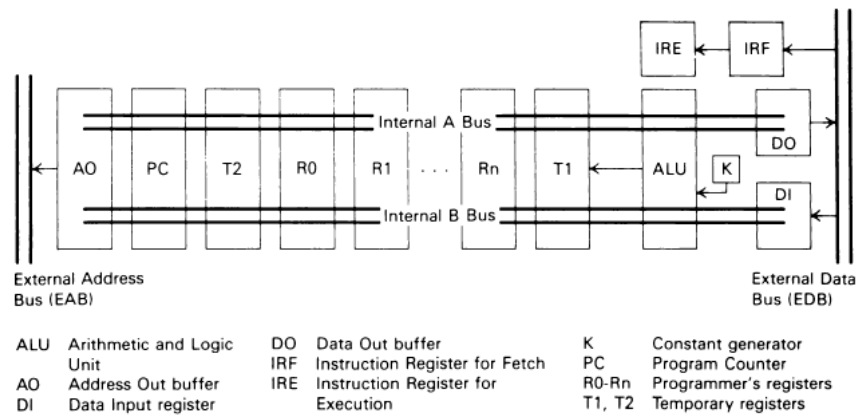**Example Rules of Operation**

1. A transfer from source to bus to destination takes one state time.
2. A source can drive up to three destination loads.
3. Inputs to the ALU are from the A (internal) bus and either K (values 0, +1, -1) or the B (internal) bus.
4. When the ALU is a destination, T1 is automatically loaded from the ALU output.
5. A transfer to AO activates the on-chip external bus controller.

Figure 3.4 MIN execution unit block diagram

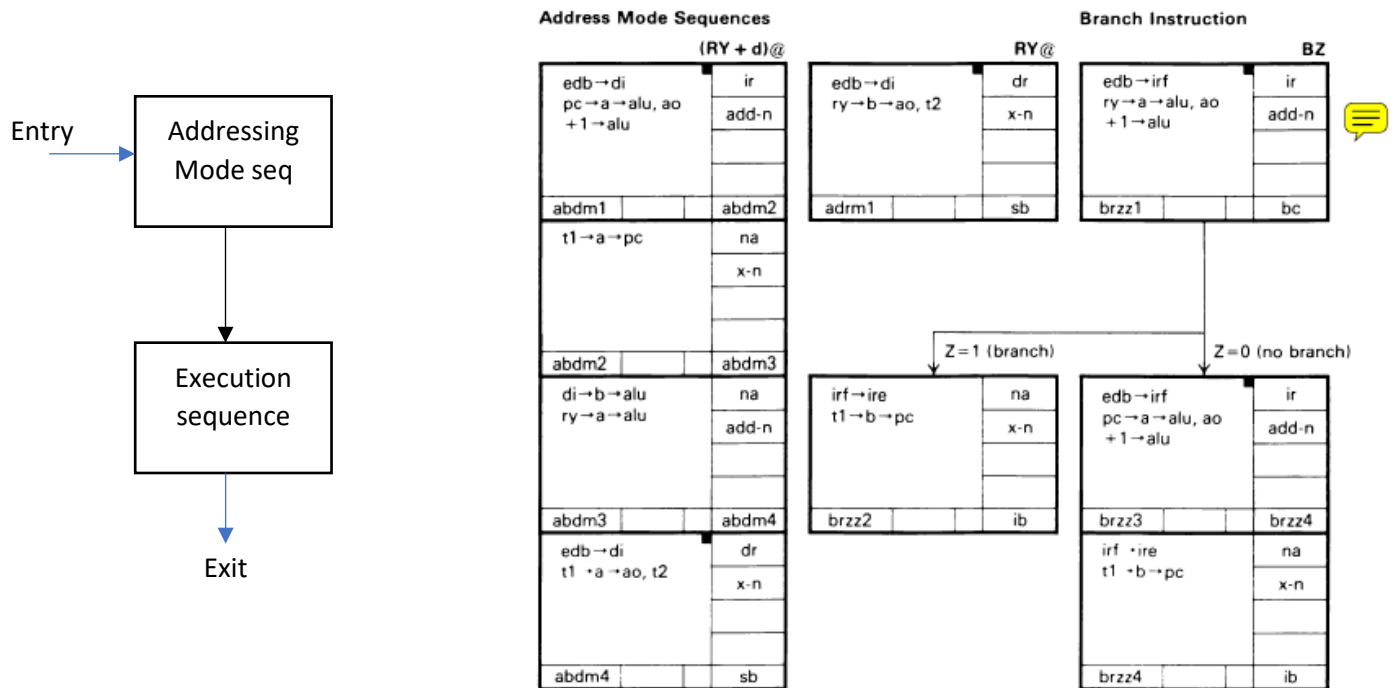Flow chart used in the project / CISC micro-code:



		bit_irelf	bit_SrcAO	bit_WriteDO	bit_DesEdb	bit_SrcABus	bit_SrcBBus	bit_SrcRx	bit_SrcRy	bit_SrcT2	bit_SrcPC	bit_2ndOperand	bit_IntExtOp	bit_flagUpdate	bit_T1Update	bit_EnableALU
		25	23:24	22	20:21	17:19	14:16	12:13	10:11	8:9	6:7	4:5	3	2	1	0
		1	2	1	2	3	3	2	2	2	2	2	1	1	1	1
	State ID	IRF→IRE	Memory Operation			Src → A Bus	Src → B Bus	Bus Destination				ALU Operation				
			Src → AO	A → DO	MEM → dest			Rx	Ry	T2	PC	2nd Operand	Int/Ext Operation	UpdateFlag	UpdateT1	EnableALU
ControlStore	XXXX	0	A → AO : 01 B → AO : 10 None : 00		edb → DI : 01 edb → IRF : 10 None : 00	Rx → A -001 Ry → A -010 T1 → A -011 T2 → A -100 PC → A -101 None : 000	Rx → B -001 Ry → B -010 T1 → B -011 T2 → B -100 PC → B -101 DI → B -110 None : 000	A → Rx : 01 B → Rx : 10 None : 00	A → Ry : 01 B → Ry : 10 None : 00	A → T2 : 01 B → T2 : 10 None : 00	A → PC : 01 B → PC : 10 None : 00	B → ALU : 00 +1 → ALU : 01 -1 → ALU : 10 0 → ALU : 11	External : 1 Internal/ADD : 0			
0	NOP	0	00	0	00	000	000	00	00	00	00	00	0	0	0	0
1	abdm1	0	01	0	01	101	000	00	00	00	00	01	0	0	1	1
2	abdm2	0	00	0	00	011	000	00	00	00	01	00	0	0	0	0
3	abdm3	0	00	0	00	010	110	00	00	00	00	00	0	0	1	1
4	abdm4	0	01	0	01	011	000	00	00	01	00	00	0	0	0	0

For each StateID, its corresponding micro-actions to take place inside EU to achieve one micro-instruction is elaborated in the spreadsheet as above. Note, the complete 36 StateIDs and its decoded control word is available in the project document (*BitFormat_ControlWordList.xlsx* file).

Sequence micro-instruction flow chart –

Execution Sequences for Register-to-Register and Special Instructions


RY → RX	LOAD	RY @ → RX RY + 1 → RY	POP	RY → 1 → RY RX → RY @	PUSH
edb → irf pc → a → alu, ao ry → b → rx, t2 + 1 → alu	ir add-x	edb → di ry → a → alu, ao + 1 → alu	dr add-n	ry → a → alu - 1 → alu	na add-n
ldrr1	ldrr2	popr1	popr2	push1	push2
irf → ire t1 → b → pc t2 → a → alu 0 → alu	na add-s	di → b → rx t1 → a → ry	na x-n	rx → a → do t1 → b → ao, ry	dw x-n
ldrr2	ib	popr2	popr3	push2	push3
		edb → irf pc → a → alu, ao + 1 → alu	ir add-n	edb → irf pc → a → alu, ao + 1 → alu	ir add-n
		popr3	popr4	push3	push4
		irf → ire t1 → b → pc	na x-n	irf → ire t1 → b → pc	na x-n
		popr4	ib	push4	ib
RX OP RY → RY	ADD, AND, SUB	RX → RY	STORE		
rx → a → alu ry → b → alu	na op-s	edb → irf pc → a → alu, ao + 1 → alu	ir add-x		
opr1	opr2	strr1	strr2		
edb → irf pc → a → alu, ao t1 → b → pc + 1 → alu	ir add-n	irf → ire t1 → b → pc t2 → a → alu 0 → alu	na add-s		
opr2	opr3	strr2	ib		
irf → ire t1 → b → pc	na x-n				
opr3	ib				

Execution Sequences with a Memory Operand Reference

MEM → RX	LOAD	RX → MEM	STORE	RX OP MEM → MEM	ADD, AND, SUB
di → b → rx, t2 edb → irf pc → a → alu, ao + 1 → alu	ir add-x	rx → a → alu, do t2 → b → ao 0 → alu	dw add-s	di → b → alu rx → a → alu	na op-s
ldrm1	ldrm2	strm1	strm2	opr1	opr2
irf → ire t1 → b → pc t2 → a → alu 0 → alu	na add-s	edb → irf pc → a → alu, ao + 1 → alu	ir add-n	t1 → a → do t2 → b → ao	dw x-n
ldrm2	ib	strm2	strm3	opr2	opr3
		irf → ire t1 → b → pc	na x-n	edb → irf pc → a → alu, ao + 1 → alu	ir add-n
		strm3	ib	opr3	opr4
		test1	test2	irf → ire t1 → b → pc	na x-n
		irf → ire t1 → b → pc t2 → a → alu 0 → alu	na add-s	opr4	ib
		test2	ib		

For each StateID, its corresponding micro-actions to take place inside EU to achieve one micro-instruction is elaborated in the spreadsheet as above. Note, the complete 36 StateIDs and its decoded control word is available in the project document (*BitFormat_ControlWordList.xlsx* file).

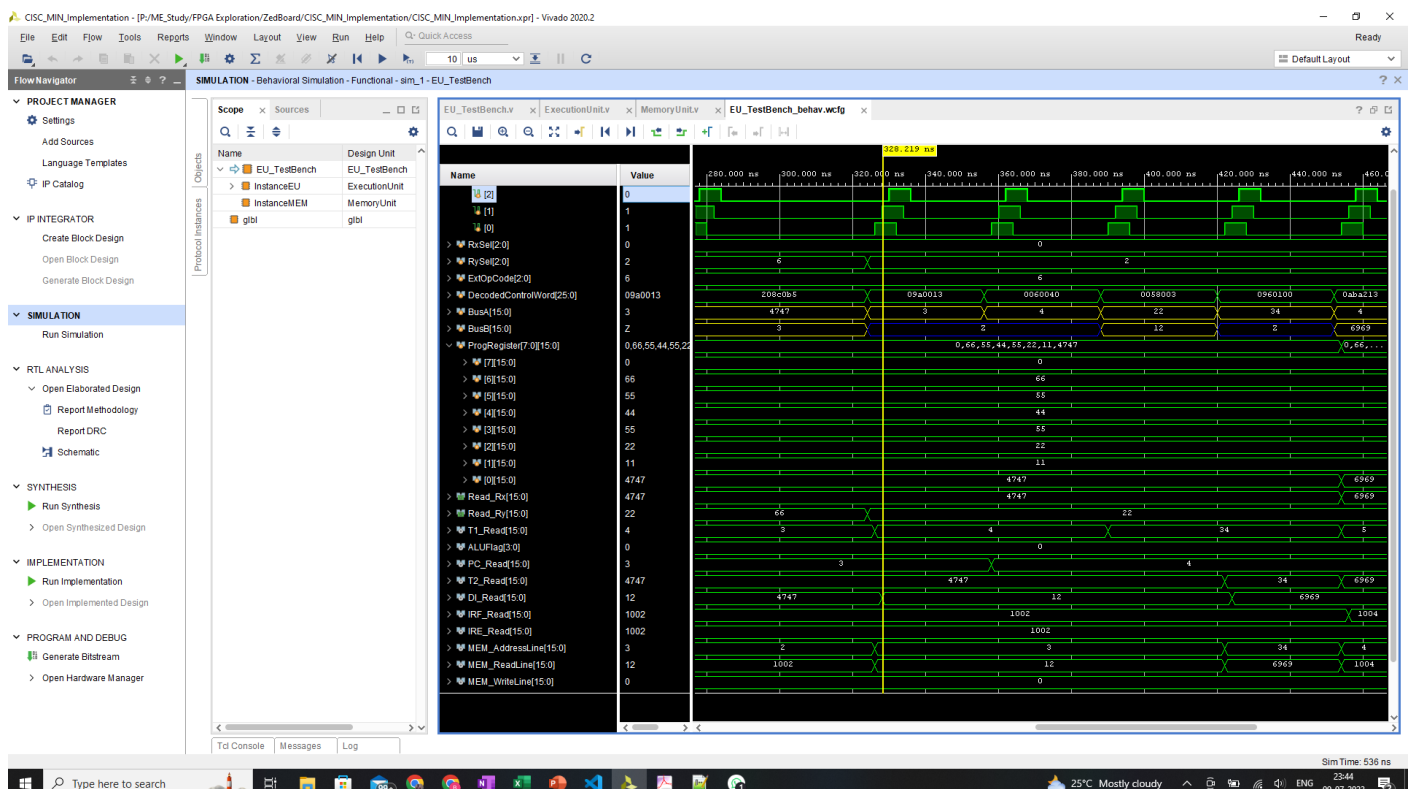Testing Data path using vivado simulation –




Control Plane Development –

The Control plane encompasses the control logic that orderly sequence the micro-code to the provided programmer's instruction, and sequence the system to read next instruction. It encompasses, Control Store Unit, Instruction decoder unit, Next State logic unit.

Instruction Decoder Unit-

This unit decodes the IRE Op-code to get details –

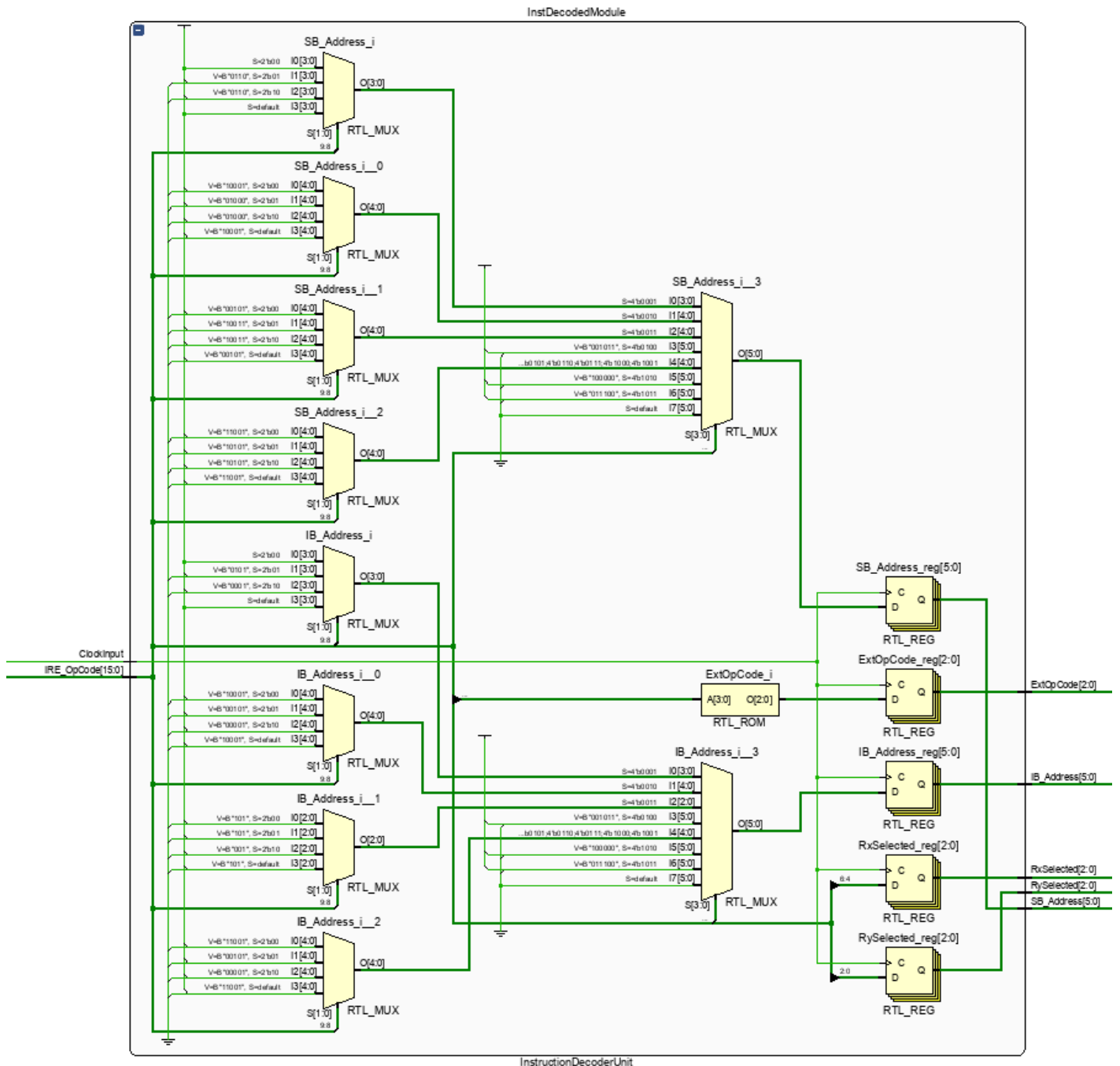- Programmer's operation to perform (ADD,LDR,TST etc.,)
- Addressing mode (direct/indirect/indirect+base)
- Selected Rx and Ry (R0-R7)




The circuit is designed in HDL and the synthesized RTL design is as above. IRE is decoded and decoded information is made available at every clock pulse.

Op Code	Instr.	Modes applicable	Inst Branch			Seq Branch			ExtOpCode
			0-direct	1-indirect	2-indirect+DP	0-direct	1-indirect	2-indirect+DP	
0	NOP	x	0	0	0	0	0	0	0
1	LDR	all	15	5	1	15	6	6	0
2	STR	all	17	5	1	17	8	8	0
3	TST	indirect only	5	5	1	5	19	19	0
4	BZ	x	11	11	11	11	11	11	0
5	ADD	all	25	5	1	25	21	21	ADD
6	SUB	all	25	5	1	25	21	21	SUB
7	AND	all	25	5	1	25	21	21	AND
8	OR	all	25	5	1	25	21	21	OR
9	XOR	all	25	5	1	25	21	21	XOR
10	PUSH	x	28	28	28	28	28	28	0
11	POP	x	32	32	32	32	32	32	0

Decoded parameters – Instruction branch, Sequence branch, External Operation, Rx and Ry selected. Above is the workout for each instruction and its corresponding IB and SB. Using this data, the Instruction decoder is designed to resolve same.

Next State Logic Unit –

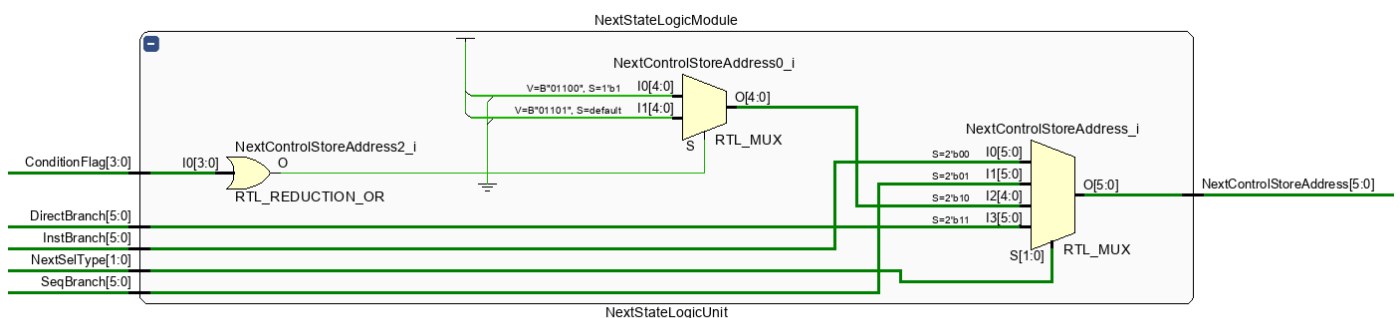This Unit is responsible to generate the Next State-ID the micro-code to move. The state could flow to either new Instruction Branch, or next execution sequence (SB), or direct branch as specified in the Control word of current micro-code, or a conditional branch i.e., BZ.



The Next State-ID / ControlStoreAddress is branched to either IB/SB/DB/conditional branch (bzrr2 if true, bzrr4 for false). Note, in this project we have zero flag CC and BZ is the only branching instruction. The detail control word will be discussed in next section.

Reference –


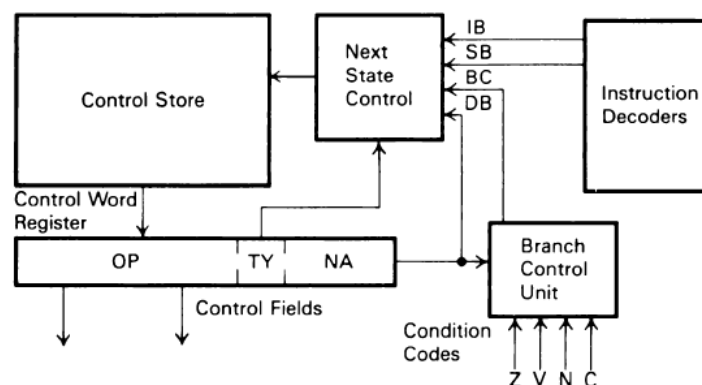


Figure 4.18 Control store branch control and next address select

Control Store Unit-

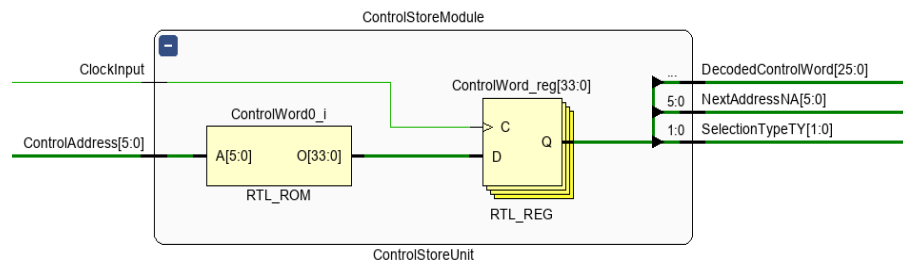

It's a ROM memory that holds the Control Word (34 bits wide) for each State-ID/Control Address. Below is the anatomy

Control Word		
26 bits	2 bits	6 bits
Decoded Control Word	TY selection	Next Address


Content stored in the Control Store –

ControlStore_Address	bits position -		33-8		7-6		5-0	
	StateID	DecodedControlWord 26 bits	NextAddressSelection		NextControlStoreAddress			
			TY - 2 bit		NA - 6 bits			
0	NOP	0x0	11		13			
1	abdm1	0x9a0013	11		2			
2	abdm2	0x60040	11		3			
3	abdm3	0x58003	11		4			
4	abdm4	0x960100	01		0			
5	adrm1	0x1108200	01		0			
6	ldrm1	0xaba213	11		7			
7	ldrm2	0x208c0b5	00		0			
8	strm1	0x1430035	11		9			
9	strm2	0xaa0013	11		10			
10	strm3	0x200c080	00		0			
11	brzz1	0xa40013	10		13			
12	brzz2	0x200c080	00		0			
13	brzz3	0xaa0013	11		14			
14	brzz4	0x200c080	00		0			
15	ldrr1	0xaaa213	11		16			
16	ldrr2	0x208c0b5	00		0			
17	strr1	0xaa4a13	11		18			
18	strr2	0x208c0b5	00		0			
19	test1	0xab8213	11		20			
20	test2	0x208c0b5	00		0			
21	oprm1	0x3800f	11		22			
22	oprm2	0x1470000	11		23			
23	oprm3	0xaa0013	11		24			
24	oprm4	0x200c080	00		0			
25	oprr1	0x2800f	11		26			
26	oprr2	0xaac093	11		27			
27	oprr3	0x200c080	00		0			
28	popr1	0x940013	11		29			
29	popr2	0x7a400	11		30			
30	popr3	0xaa0013	11		31			
31	popr4	0x200c080	00		0			
32	push1	0x40023	11		33			
33	push2	0x142c800	11		34			
34	push3	0xaa0013	11		35			
35	push4	0x200c080	00		0			

Testing Control Plane using Vivado Simulation –

ASM code	Nibble-3	Nibble-2	Nibble-1	Nibble-0	OpCode	MicroCode (StateID) flow	TEST
NOP	0	0	-	-	16'h0000	0,13,14	Pass
LDR RX,RY	1	0	*Rx	*Ry	16'h1021	15,16	Pass
LDR RX,[RY]	1	1	*Rx	*Ry	16'h1121	5,6,7	Pass
LDR RX,[RY+DP]	1	2	*Rx	*Ry	16'h1221	1,2,3,4,6,7	Pass
BZ RY	4	0	-	*Ry	16'h4001	11,12(branch) or 11,13,14(no)	Pass
STR RX,RY	2	0	*Rx	*Ry	16'h2021	17,18	Pass
STR RX,[RY]	2	1	*Rx	*Ry	16'h2121	5,8,9,10	Pass
STR RX,[RY+DP]	2	2	*Rx	*Ry	16'h2221	1,2,3,4,8,9,10	Pass
TST [RY]	3	1	-	*Ry	16'h3101	5,19,20	Pass
TST [RY+DP]	3	2	-	*Ry	16'h3201	1,2,3,4,19,20	Pass
ADD RX,RY	5-9**	0	*Rx	*Ry	16'h5021	25,26,27	Pass
ADD RX,[RY]	5-9**	1	*Rx	*Ry	16'h5121	5,21,22,23,24	Pass
ADD RX,[RY+DP]	5-9**	2	*Rx	*Ry	16'h5221	1,2,3,4,21,22,23,24	Pass
PUSH RX,RY	A	0	*Rx	*Ry	16'hA021	32,33,34,35	Pass
POP RX,RY	B	0	*Rx	*Ry	16'hB021	28,29,30,31	Pass
** ADD=5 SUB=2..XOR=9 *Rx = 2, Ry = 1							

LDR R4, [R5+DP] testing the sequence -

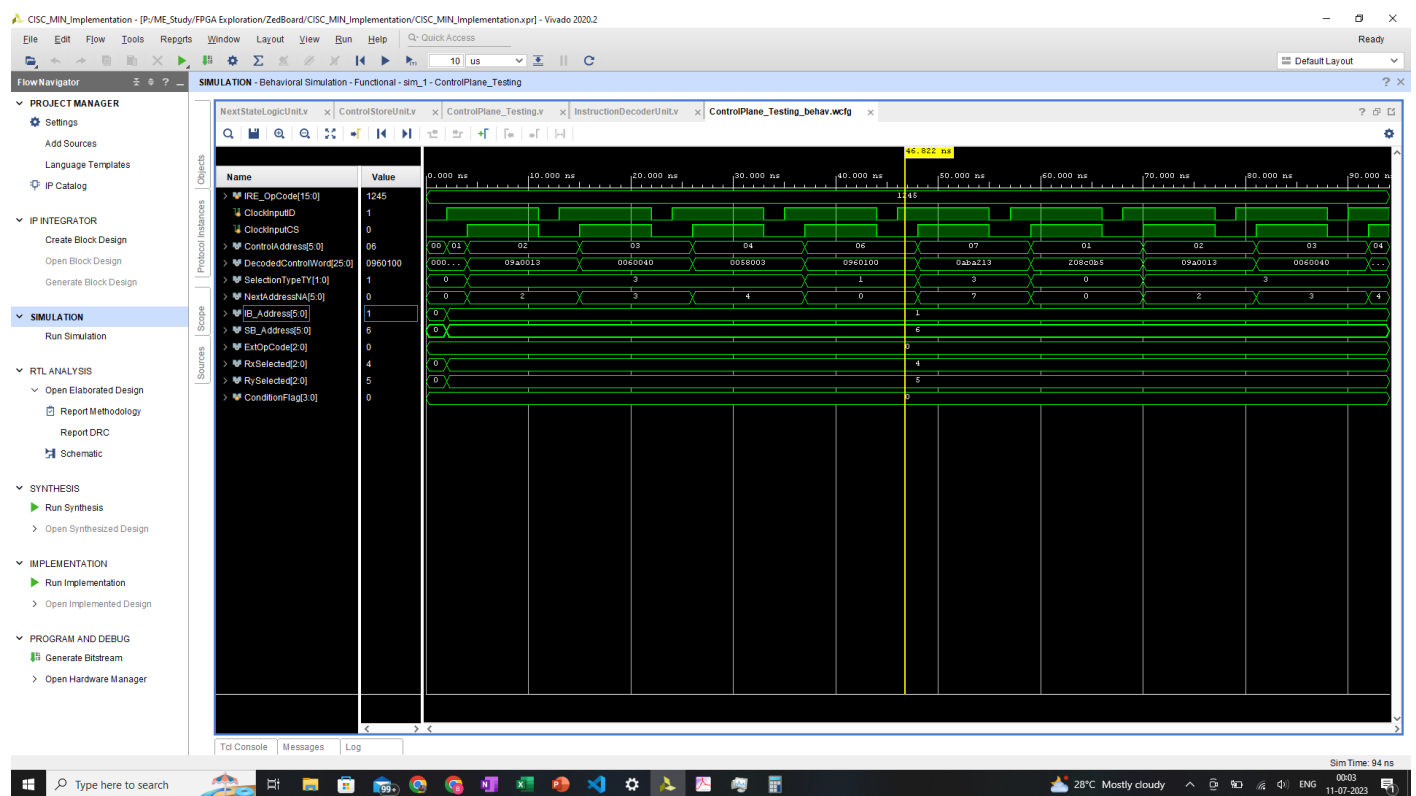

Overall Unit integration and RTL analysis –

The detailed source code and testbench code are available in the drive resource.


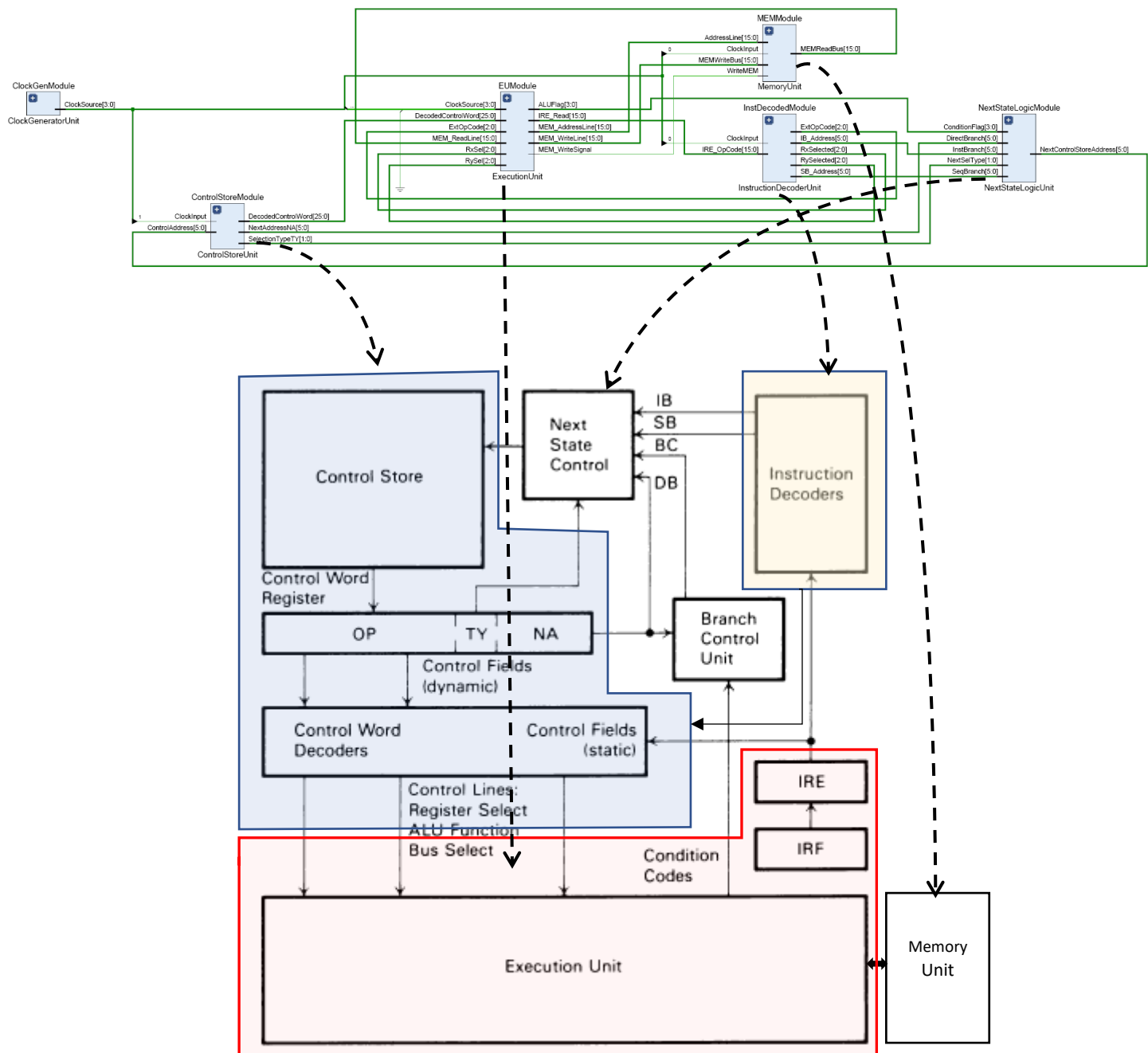


Figure 4.1 Microprocessor block diagram (microcoded controller)

Testing Programmer's instruction –

Address	Operation	at end	OpCode	
0	NOP	200,66,55,44,33,22,11,0	16'h0000	MemoryBank[0]=16'h0000;
1	LDR R5,R7	200,66,200,44,33,22,11,0	16'h1057	MemoryBank[1]=16'h1057;
2	LDR R4,[R5]	200,66,200,10,33,22,11,0	16'h1145	MemoryBank[2]=16'h1145;
3	LDR R6,[R7+10]	200,57,200,10,33,22,11,0	16'h1267	MemoryBank[3]=16'h1267;
4			16'hA	MemoryBank[4]=16'hA;
5	STR R3,[R7]	200,57,200,10,33,22,11,0	16'h2137	MemoryBank[5]=16'h2137;
6	LDR R0,[R7]	200,57,200,10,33,22,11,33	16'h1107	MemoryBank[6]=16'h1107;
7	STR R6,[R7+100]	200,57,200,10,33,22,11,33	16'h2267	MemoryBank[7]=16'h2267;
8			16'h64	MemoryBank[8]=16'h64;
9	NOP	200,57,200,10,33,22,11,33	16'h0000	MemoryBank[9]=16'h0000;
10	LDR R0,[R7+100]	200,57,200,10,33,22,11,57	16'h1207	MemoryBank[10]=16'h1207;
11			16'h64	MemoryBank[11]=16'h64;
12	ADD R0,R3 : R3<-R0+R3	200,57,200,10,90,22,11,57	16'h5003	MemoryBank[12]=16'h5003;
13	SUB R0,R4	200,57,200,47,90,22,11,57	16'h6004	MemoryBank[13]=16'h6004;
14	SUB R0,[R7]	200,57,200,47,90,22,11,57	16'h6107	MemoryBank[14]=16'h6107;
15	LDR R0,[R7]	200,57,200,47,90,22,11,24	16'h1107	MemoryBank[15]=16'h1107;
16	XOR R0,[R7+100]	200,57,200,47,90,22,11,24	16'h9207	MemoryBank[16]=16'h9207;
17			16'h64	MemoryBank[17]=16'h64;
18	LDR R0,[R7+100]	200,57,200,47,90,22,11,33	16'h1207	MemoryBank[18]=16'h1207;
19			16'h64	MemoryBank[19]=16'h64;
20	LDR R0,R7	200,57,200,47,90,22,11,200	16'h1007	MemoryBank[20]=16'h1007;
21	ADD R7,R0	200,57,200,47,90,22,11,400	16'h5070	MemoryBank[21]=16'h5070;
22	PUSH R1,R0	200,57,200,47,90,22,11,399	16'hA010	MemoryBank[22]=16'hA010;
23	PUSH R4,R0	200,57,200,47,90,22,11,398	16'hA040	MemoryBank[23]=16'hA040;
24	POP R6,R0	200,47,200,47,90,22,11,399	16'hB060	MemoryBank[24]=16'hB060;
25	POP R6,R0	200,11,200,47,90,22,11,400	16'hB060	MemoryBank[25]=16'hB060;
26	SUB R0,R7	200,11,200,47,90,22,11,400	16'h6007	MemoryBank[26]=16'h6007;
27	BZ R3	200,11,200,47,90,22,11,400	16'h4003	MemoryBank[27]=16'h4003;
28	SUB R5,R7	0,11,200,47,90,22,11,400	16'h6057	MemoryBank[28]=16'h6057;
29	BZ R3		16'h4003	MemoryBank[29]=16'h4003;
30	NOP		16'h0000	MemoryBank[30]=16'h0000;
90	LDR R0,R7	200,11,200,47,90,22,11,200	16'h1007	MemoryBank[90]=16'h1007;

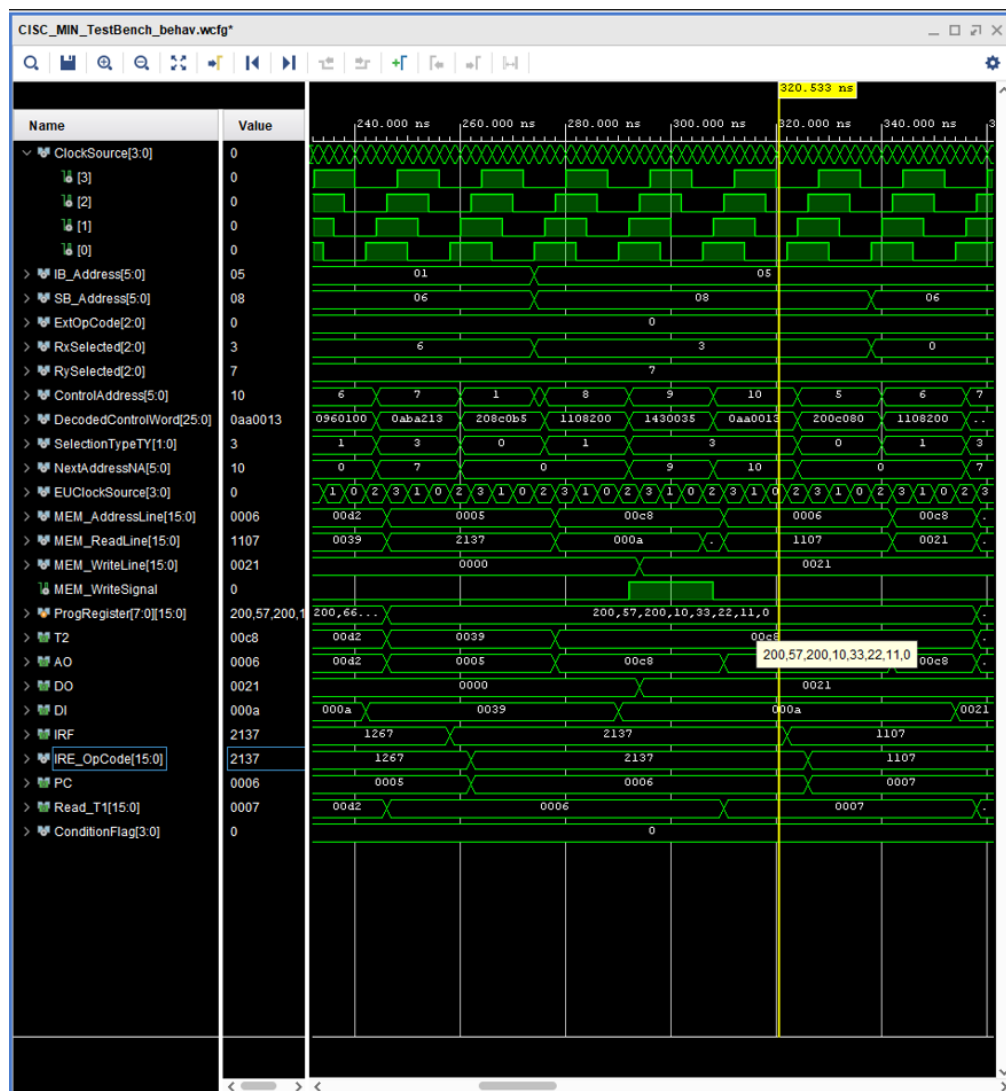



Coding Fibonacci series generator for the built microprocessor-


Address	Program for Fibanacchi series	Comment	OpCode
0	NOP		16'h0000
1	<BEGIN>: ADD R0,R6	R6<-R0+R6	16'h5006
2	ADD R1,R6	R6<-R1+R6	16'h5016
3	LDR R2,R6	R2<-R6	16'h1026
4	SUB #233,R6		16'h6076
5	BZ <RESET>	If R6==233 MAX GOTO RESET	16'h4004
6	LDR R0,R1	R0=R1	16'h1001
7	LDR R1,R2	R1=R2	16'h1012
8	SUB R6,R6	R6=0	16'h6066
9	BZ <BEGIN>	JUMP TO BEGIN	16'h4003
10	NOP		16'h0000
11	<RESET>: LDR R1,#1	R1=1	16'h1015
12	SUB R0,R0	R0=0	16'h6000
13	BZ <BEGIN>		16'h4003

Initialise registers		
R0	0	<prev prev>
R1	1	<previous>
R2	1	<output>
R3	1	<BEGIN>
R4	11	<RESET>
R5	1	#1
R6	0	<TEMP VAR>
R7	233	#233


Flowchart-

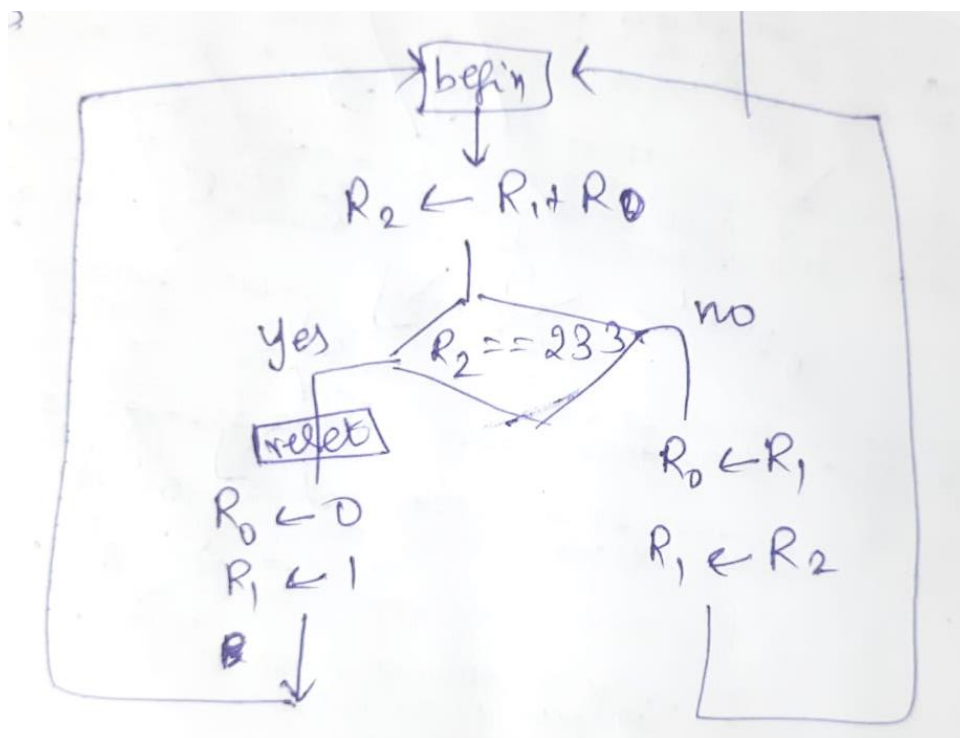

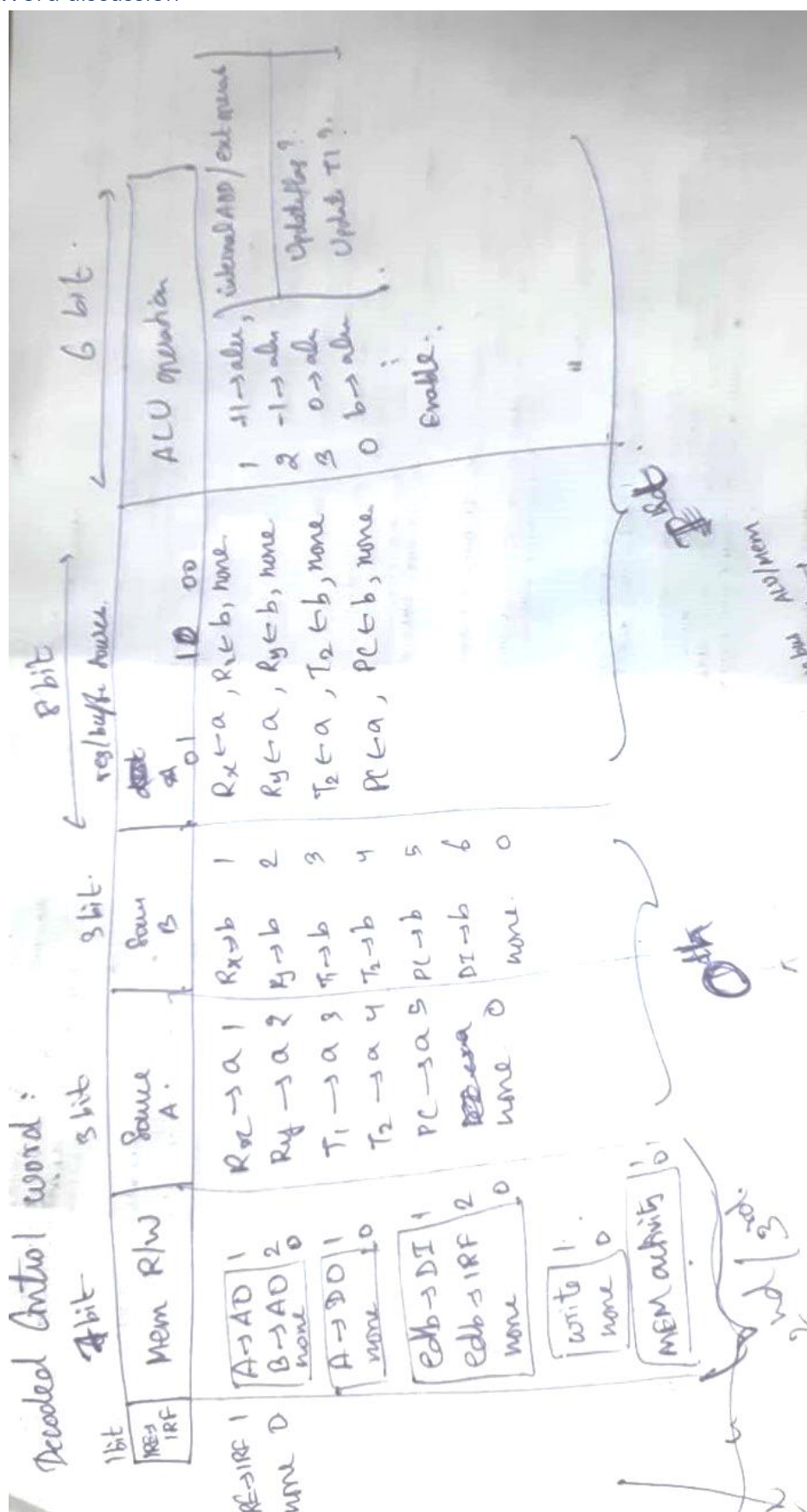


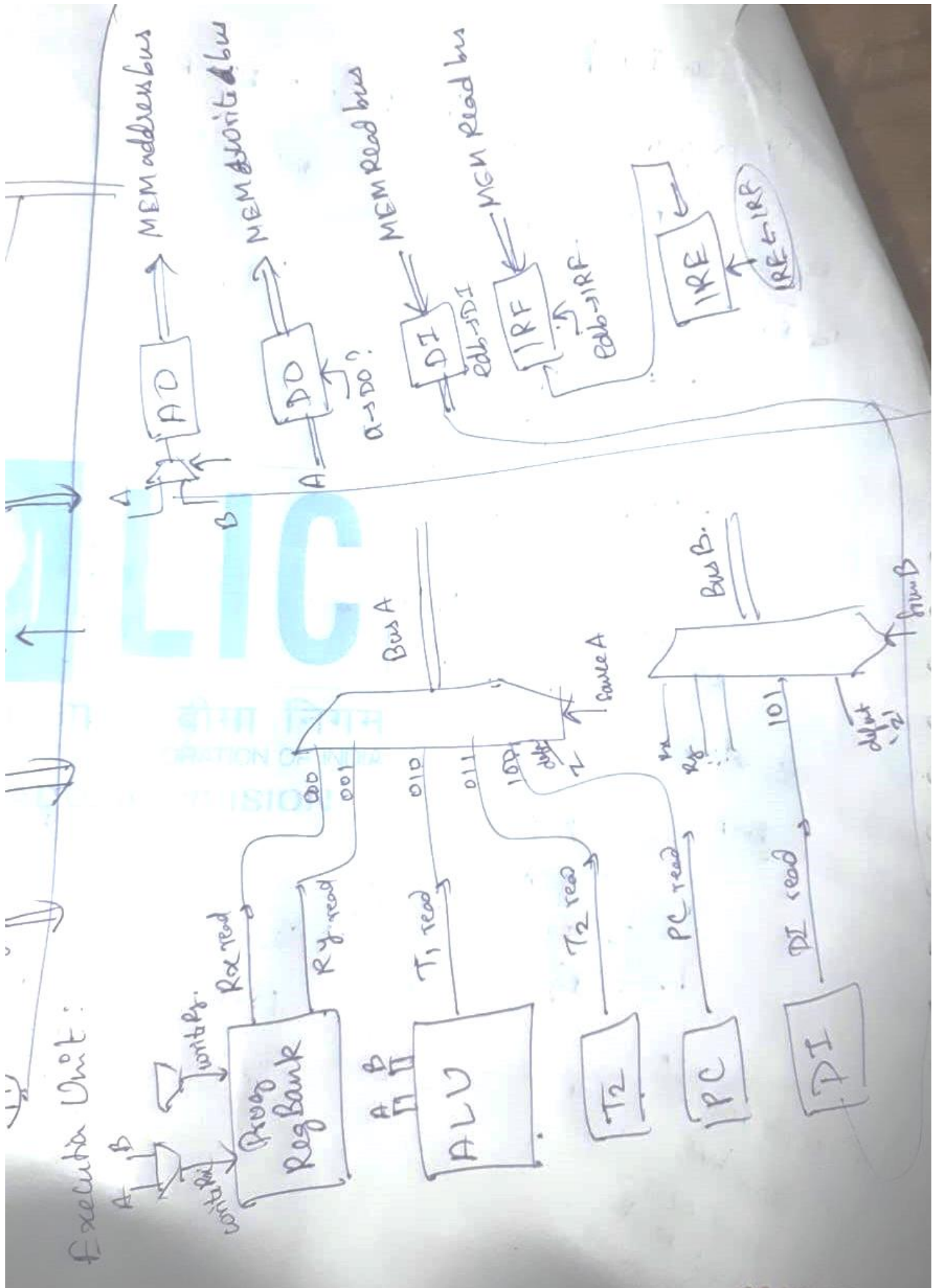

Next State logic discussion –

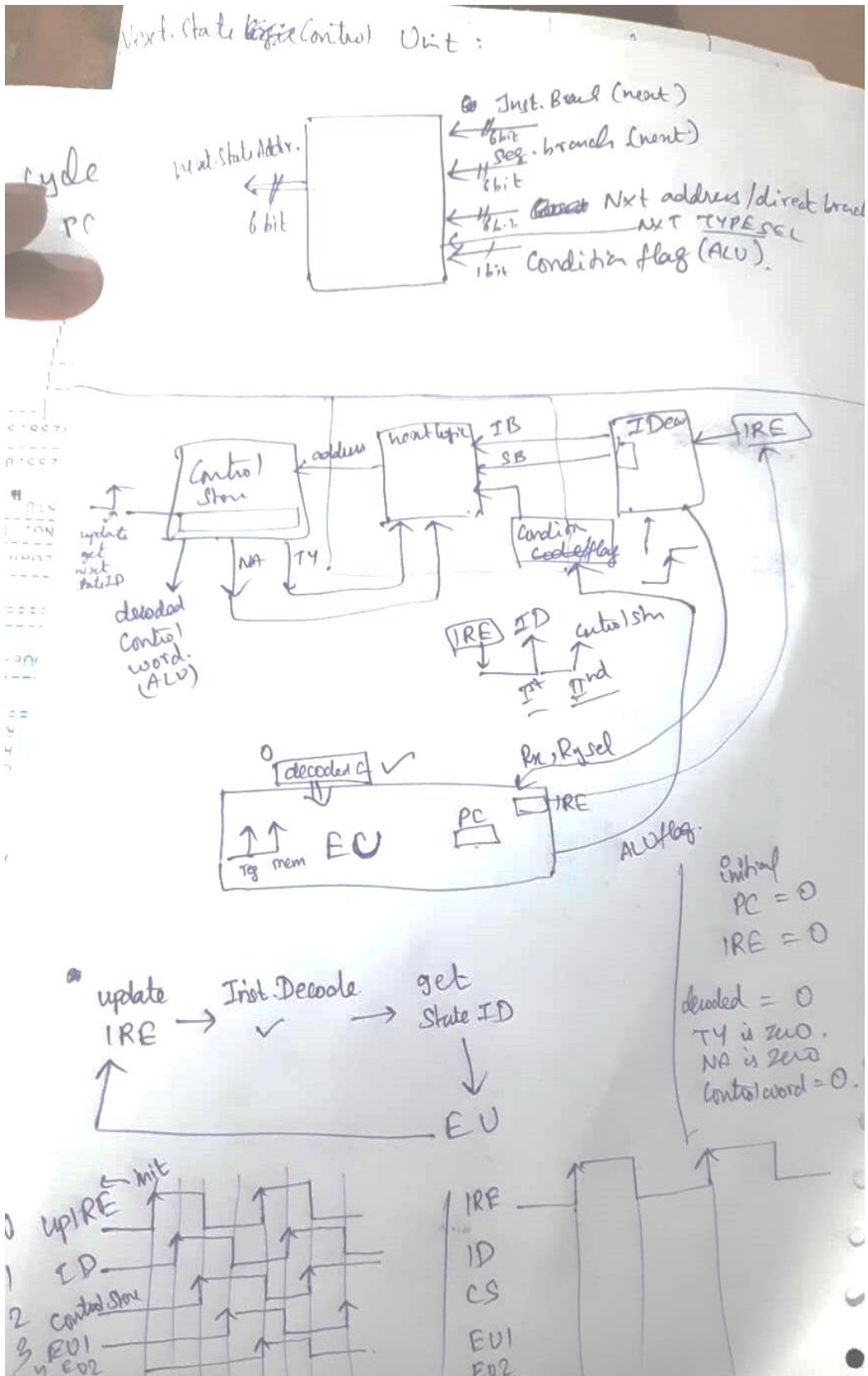

Clock Phase discussion –

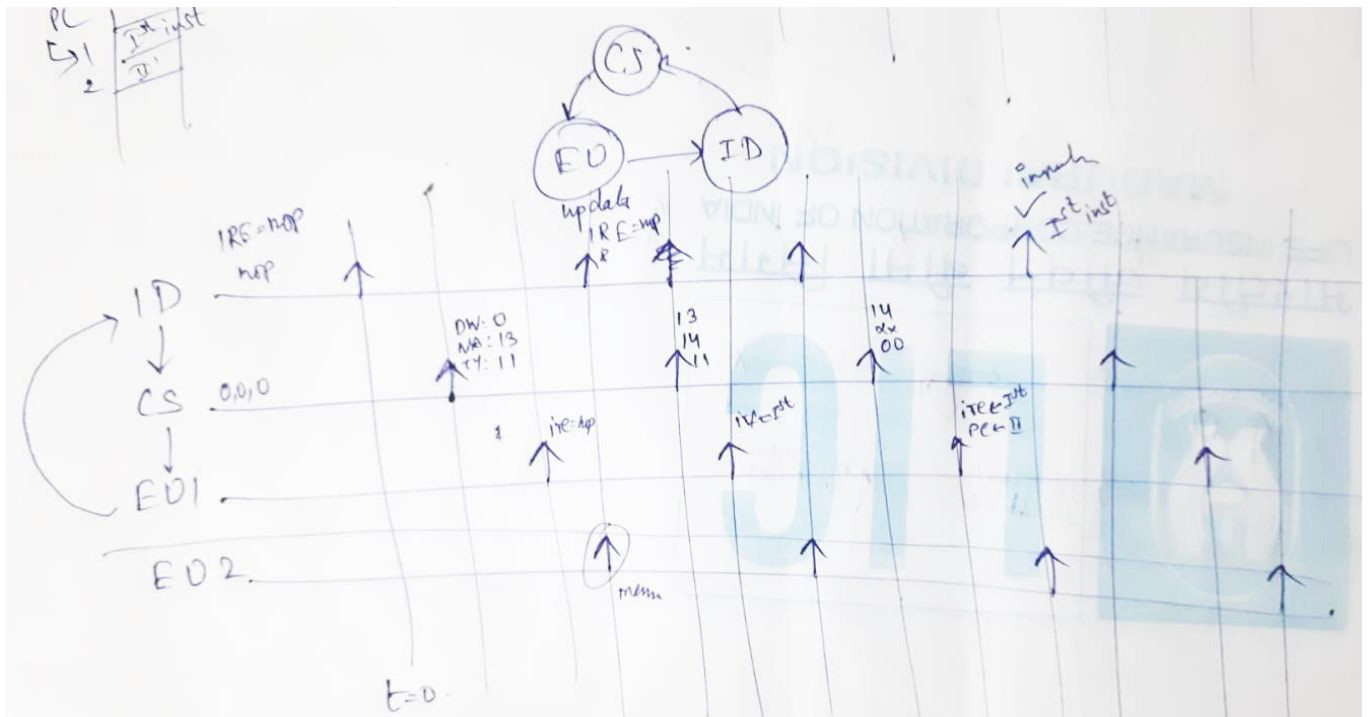

Fibonacci result –



Note - R2 register holds the result (1,2,3,5...233).

